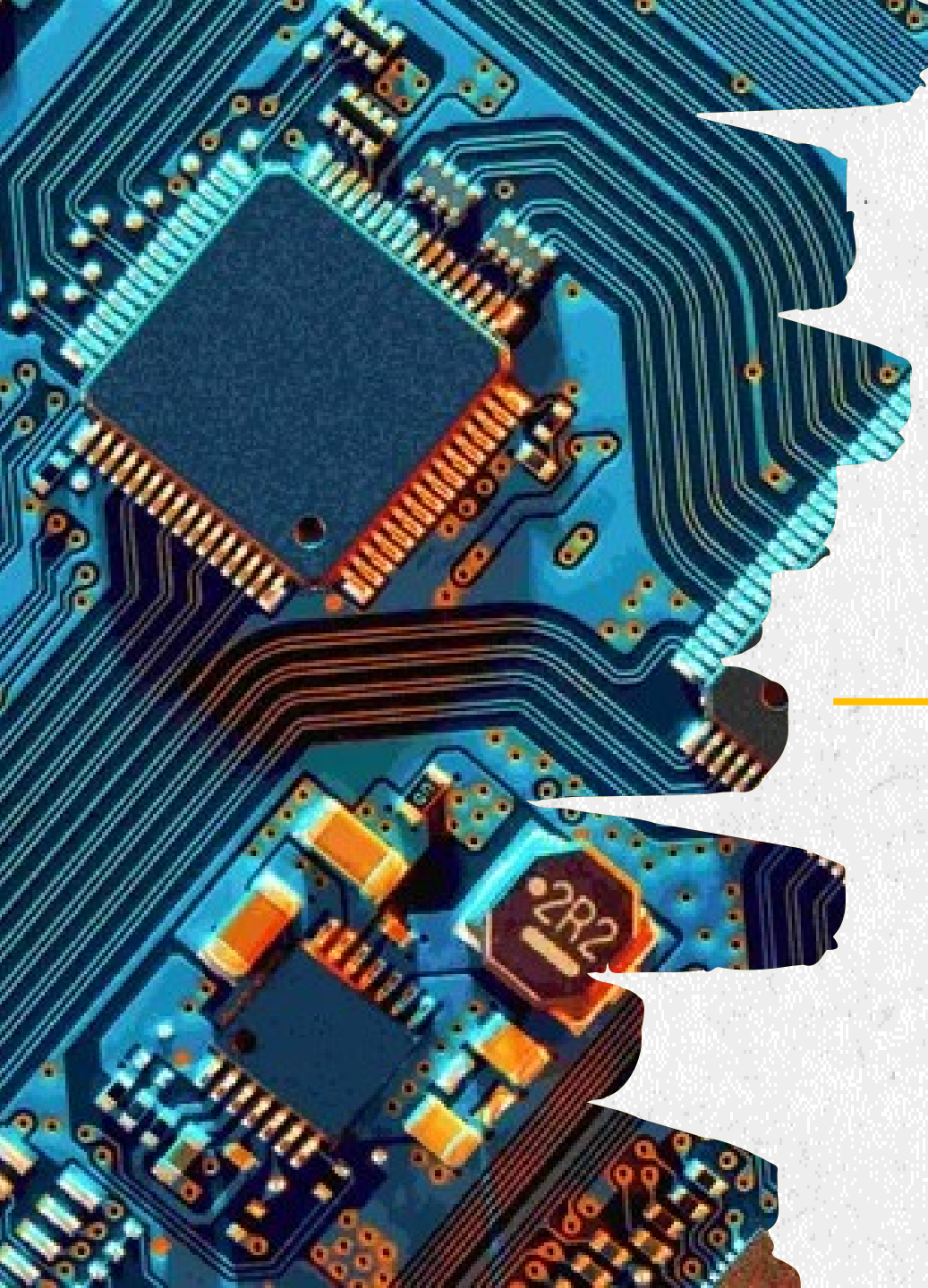






CHAPTER 7


BJT AMPLIFIERS

BJT AMPLIFIERS

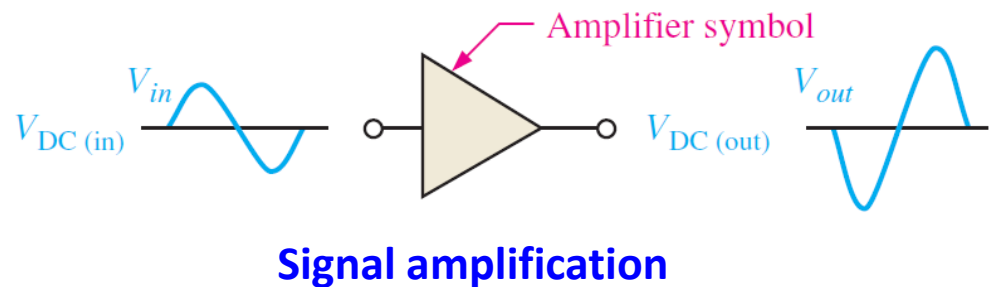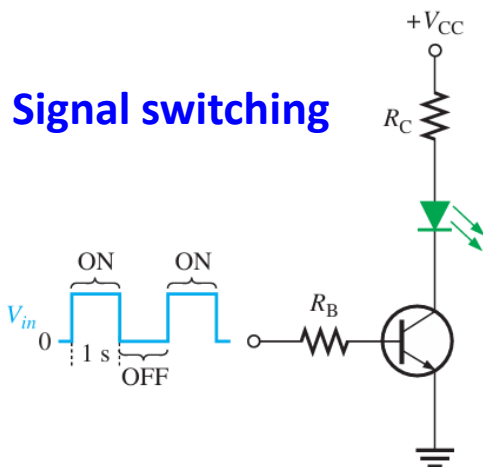- As reviewed in the previous Chapter, BJTs can be applied for two basic applications:
 1. Signal switching 訊號開關 – to use a small signal to control BJTs as a switch: on (saturation)/off (cutoff).
 2. Signal amplification 訊號放大 – to *amplify a small signal into a magnified signal* at the output port. This will be discussed more details in this Chapter.





VOLTAGE-DIVIDER BIAS

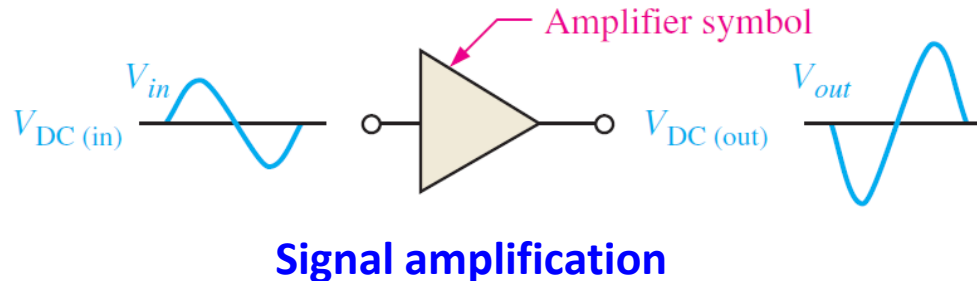

- BJTs work very well with the *positive input signal* (forward biased), while the *negative signal is blocked due to the reverse bias.*
 - To amplify the signal by BJTs,
 1. Add an DC offset to the AC input signal, such that signal is all positive!
 2. Amplify the (DC+AC) signal
 3. Filter out the DC signal, remaining the amplified AC signal
- *Voltage-divider (電壓分配) bias* – how to add up and analyze the DC offset.

DC LOAD LINE

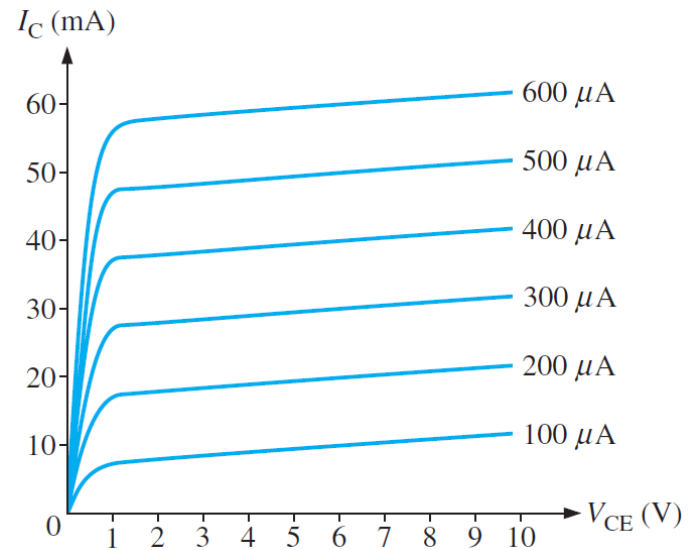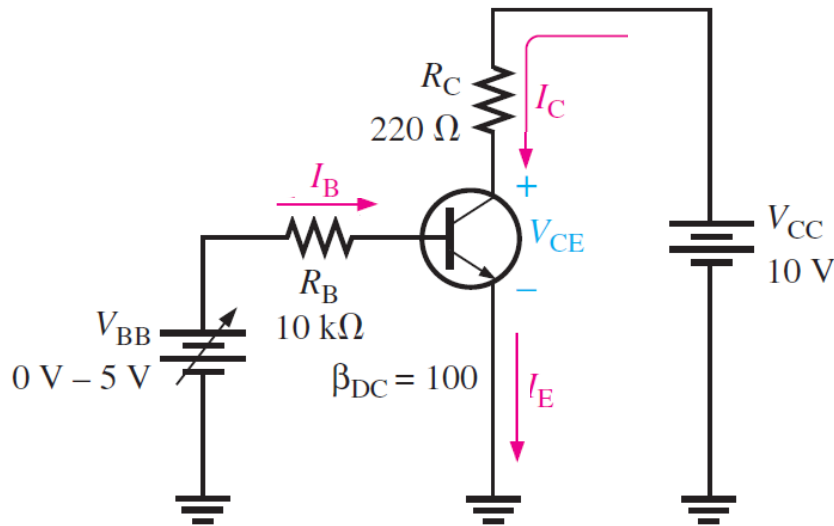



- Recall the basic BJT circuit, let us fix V_{CC} and vary V_{BB} .

Set V_{BB} such that $I_B = 200 \mu\text{A}$

$$I_C = \beta_{DC} I_B = 20 \text{ mA}$$

$$V_{CE} = V_{CC} - I_C(220)$$

$$V_{CE} = 5.6 \text{ V}$$

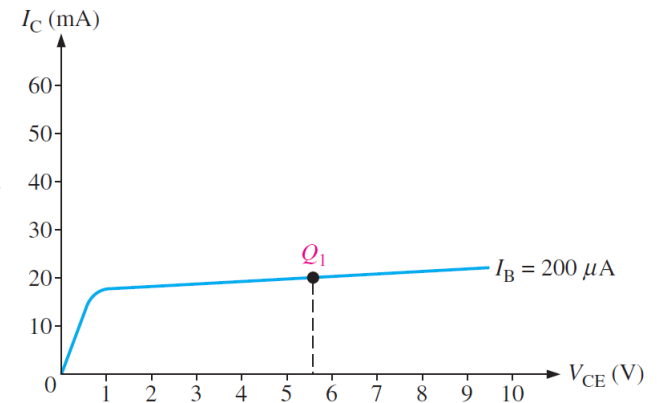
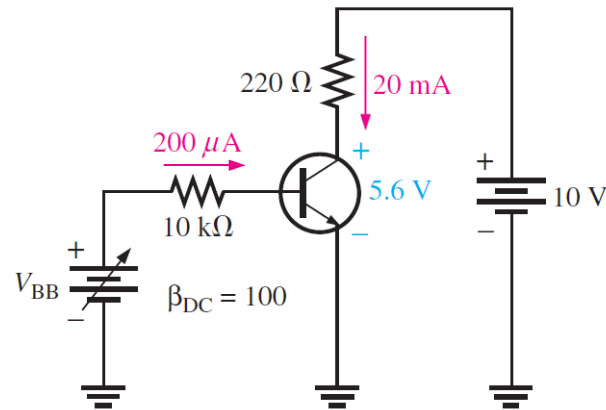


Set V_{BB} such that $I_B = 300 \mu\text{A}$

$$I_C = \beta_{DC} I_B = 30 \text{ mA}$$

$$V_{CE} = V_{CC} - I_C(220)$$

$$V_{CE} = 3.4 \text{ V}$$

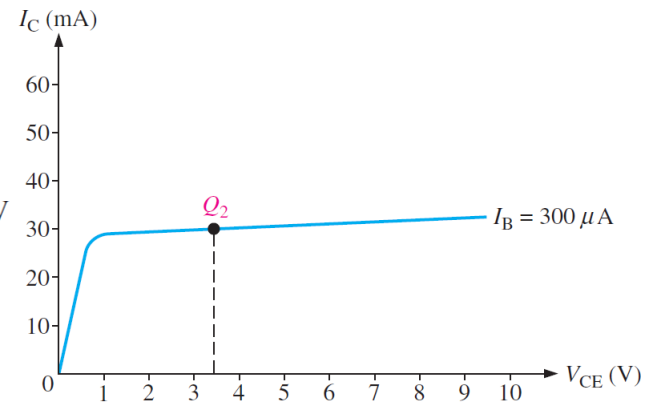
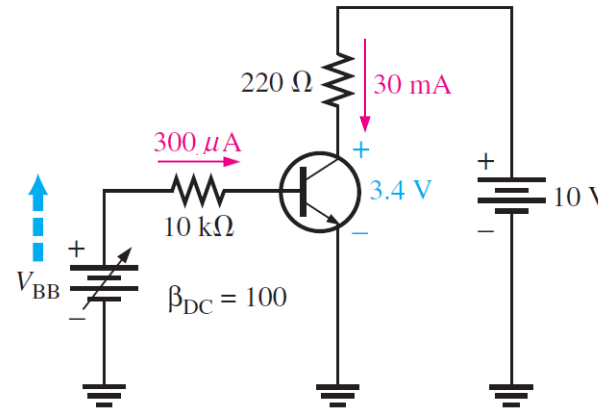


Set V_{BB} such that $I_B = 400 \mu\text{A}$




$$I_C = \beta_{DC} I_B = 40 \text{ mA}$$

$$V_{CE} = V_{CC} - I_C(220)$$

$$V_{CE} = 1.2 \text{ V}$$

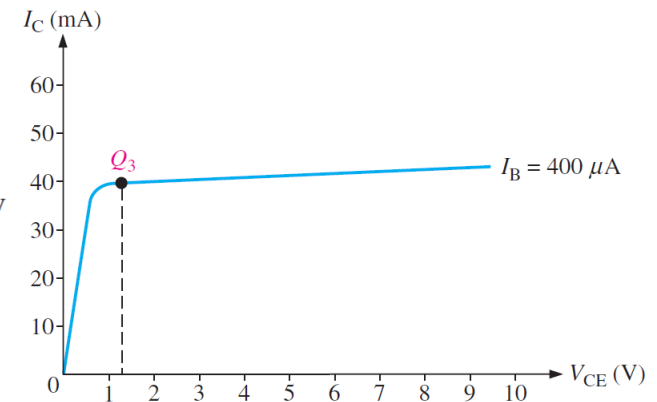
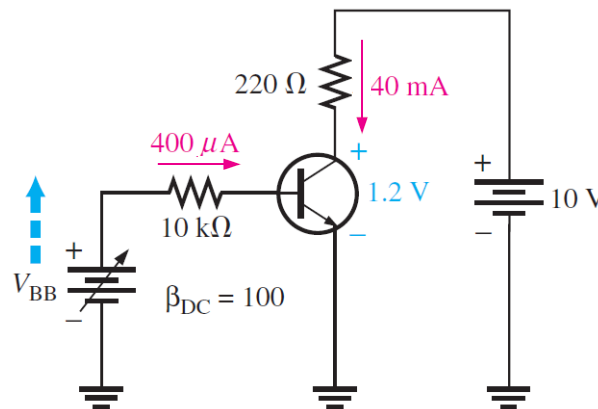


DC LOAD LINE

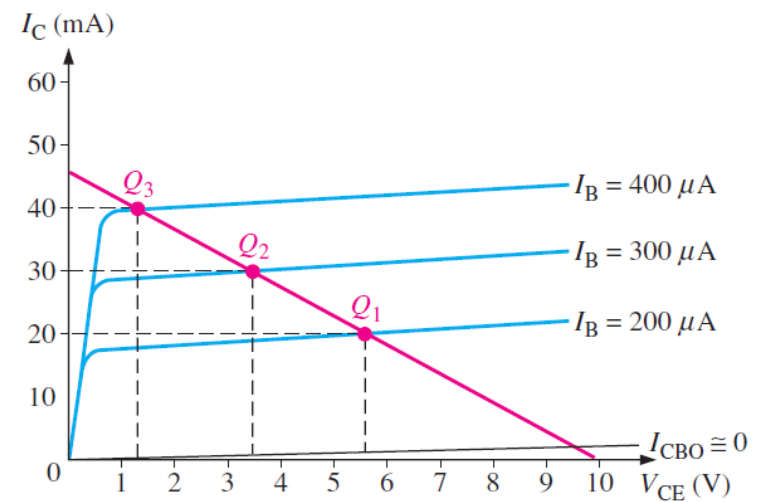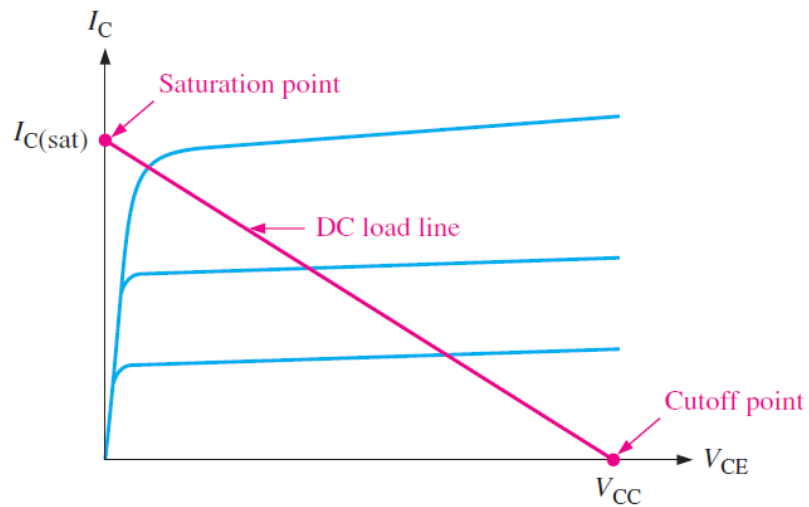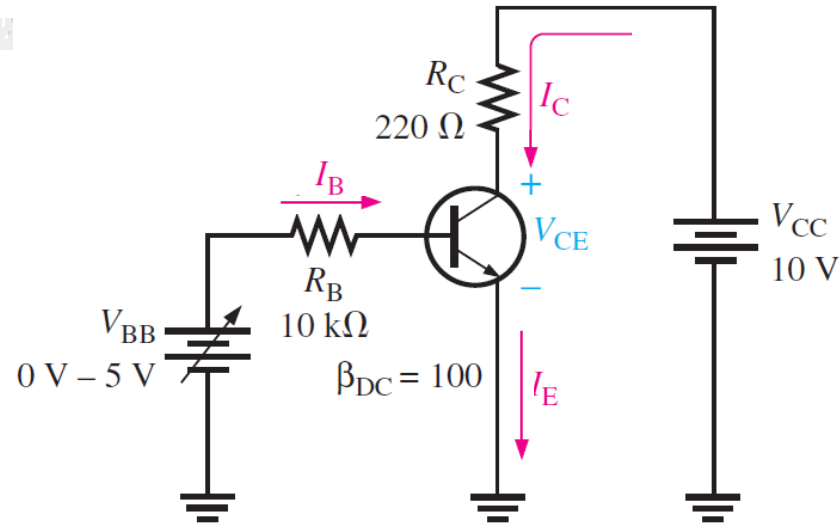

BJT WITH AC SIGNAL

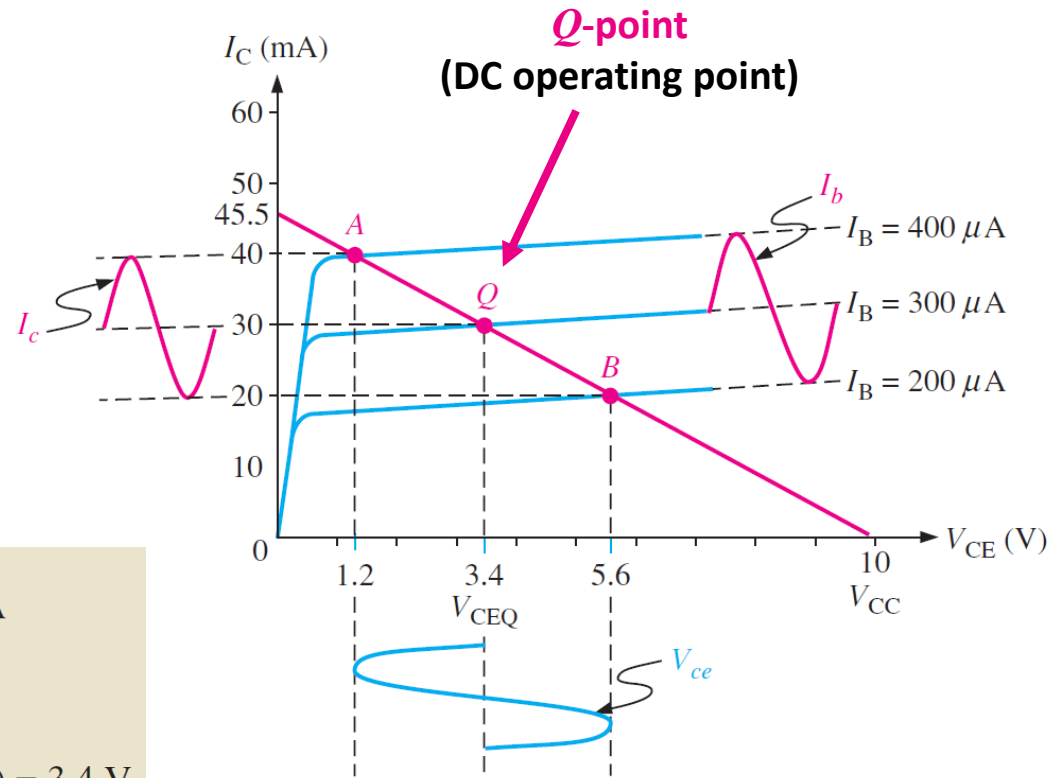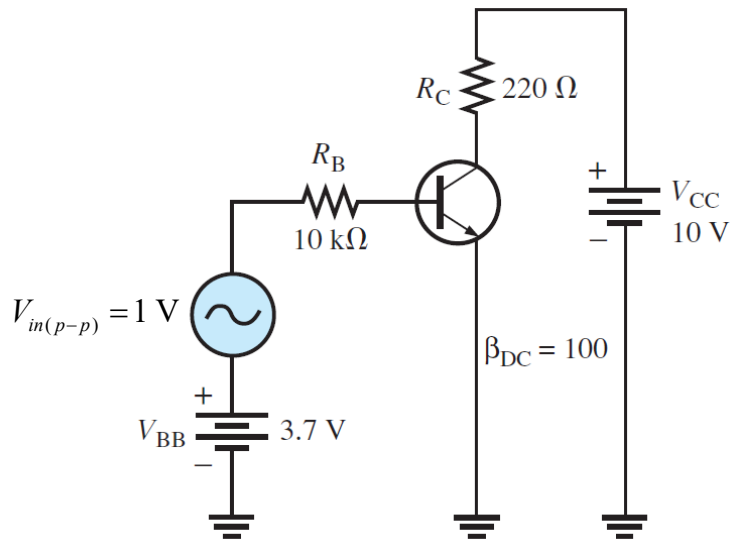- Let us add an AC signal on the DC signal V_{BB} .




$$I_{BQ} = \frac{V_{BB} - 0.7 \text{ V}}{R_B} = \frac{3.7 \text{ V} - 0.7 \text{ V}}{10 \text{ k}\Omega} = 300 \mu\text{A}$$


$$I_{CQ} = \beta_{DC} I_{BQ} = (100)(300 \mu\text{A}) = 30 \text{ mA}$$

$$V_{CEQ} = V_{CC} - I_{CQ} R_C = 10 \text{ V} - (30 \text{ mA})(220 \Omega) = 3.4 \text{ V}$$


WAVEFORM DISTORTION

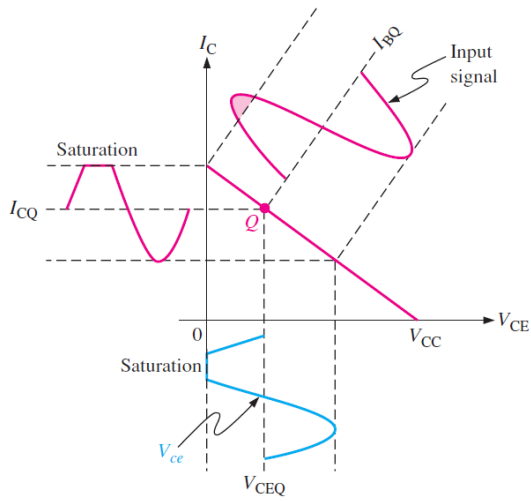

Q -point is too close to saturation.

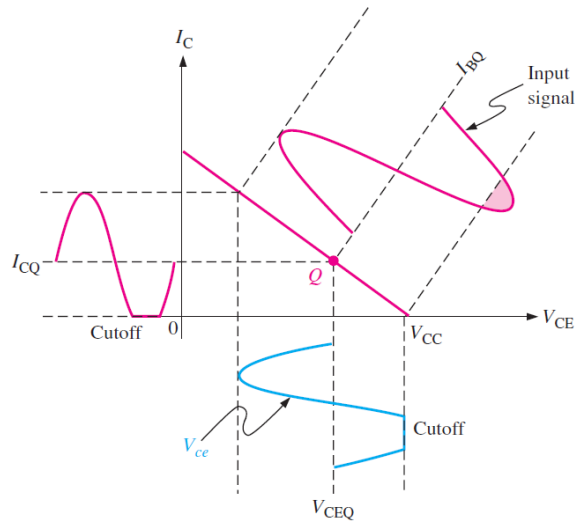


Q -point is too close to cutoff.

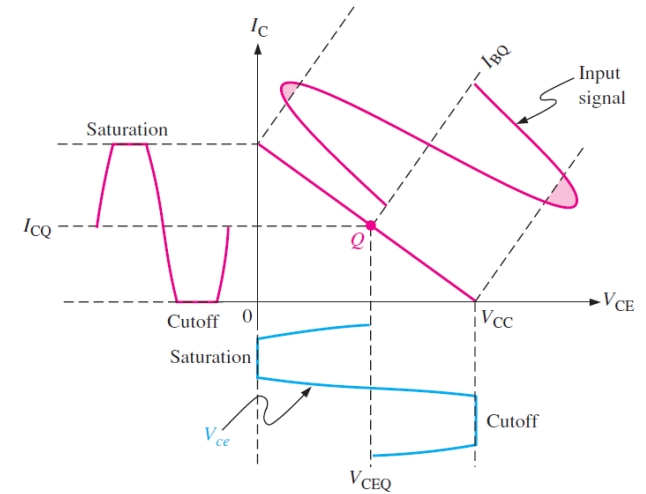

Input signal is too large.


*"These three reasons make the amplified waveform **clipped**."*

BJT AMPLIFIERS FOR AC SIGNALS

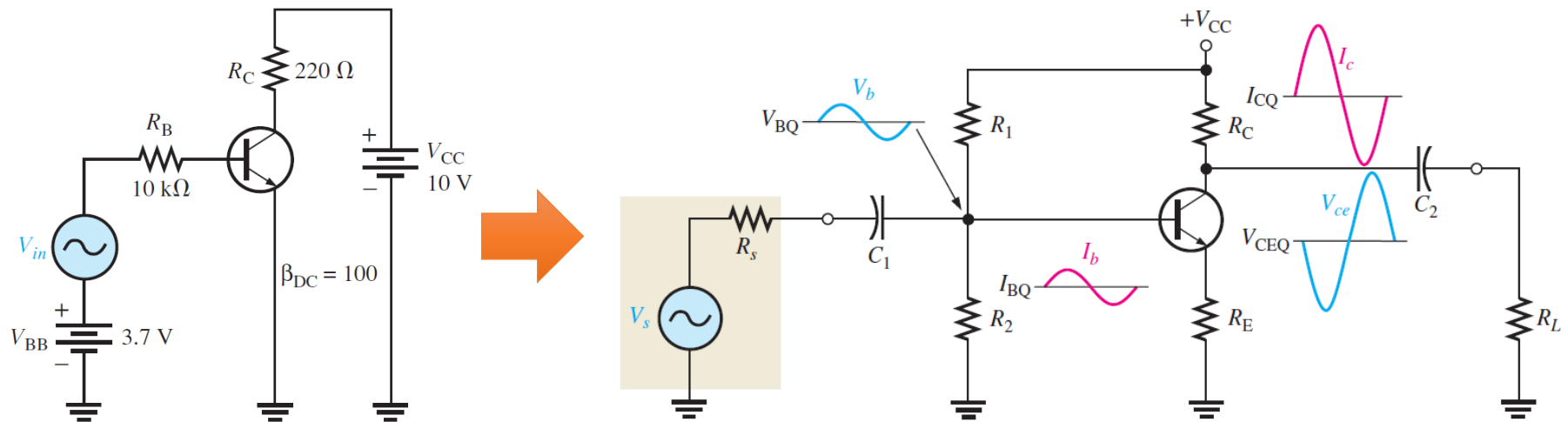

- V_s is the **input AC signal to be amplified**.
- V_{CC} is the **one and only DC voltage supply**.
- Capacitors C_1 and C_2 are to block DC currents not to flow to V_s and R_L sides, simplifying the circuit analysis.

ANALYSIS OF BJT AMPLIFIERS

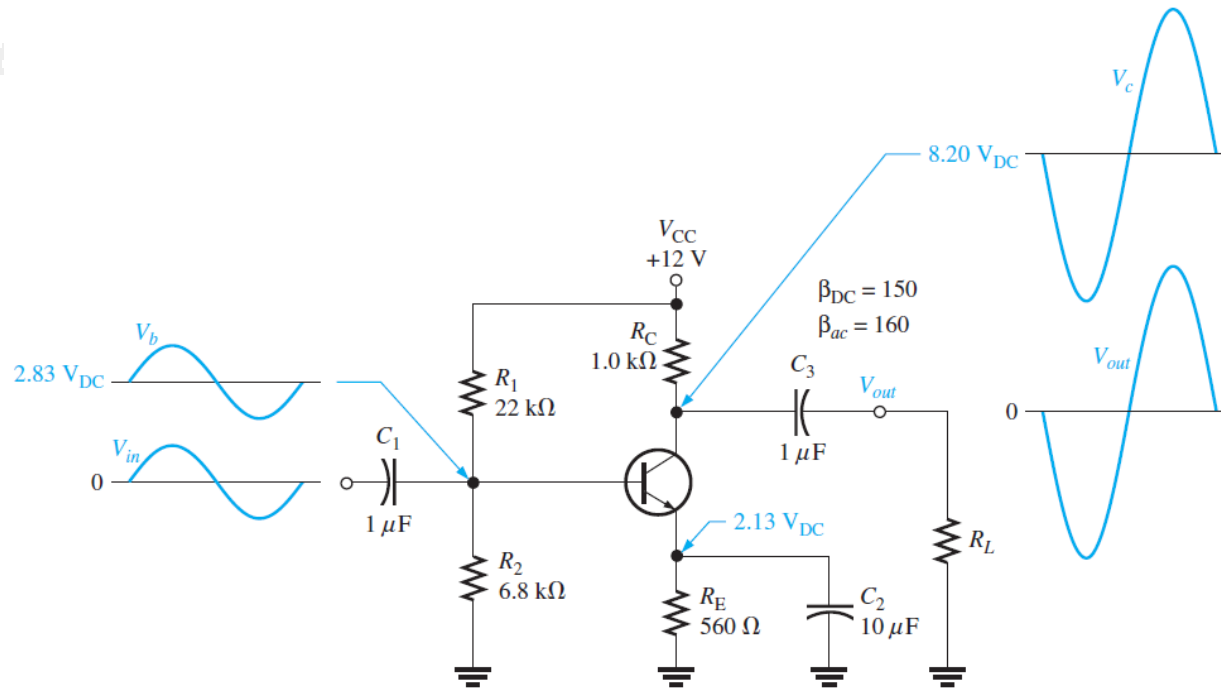

- To analyze this BJT amplifier, we split into 2 analyses:
 1. DC analysis
 2. AC analysis

APPLICATIONS

