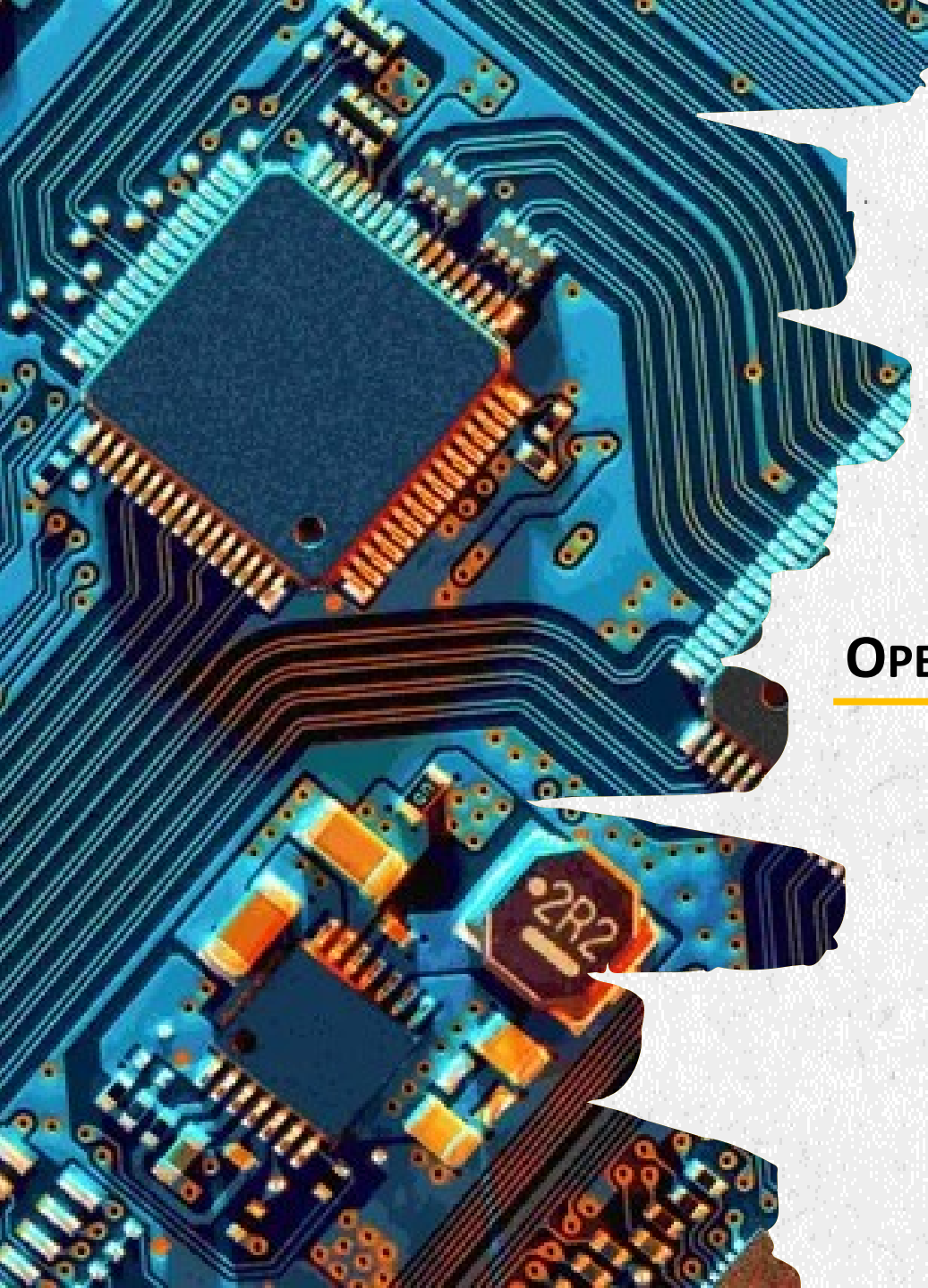





CHAPTER 9

OPERATIONAL AMPLIFIER (OP-AMP)



INTRODUCTION

- In the previous chapters, you have studied discrete components 離散元件, i.e., resistors, capacitors, inductors, diodes, and transistors. They must be interconnected in a circuit with other devices to form a complete functional unit.
- Now, we will begin the study of integrated circuits (ICs、積體電路), where many resistors, capacitors, diodes, transistors are embedded on a single tiny chip 晶片.

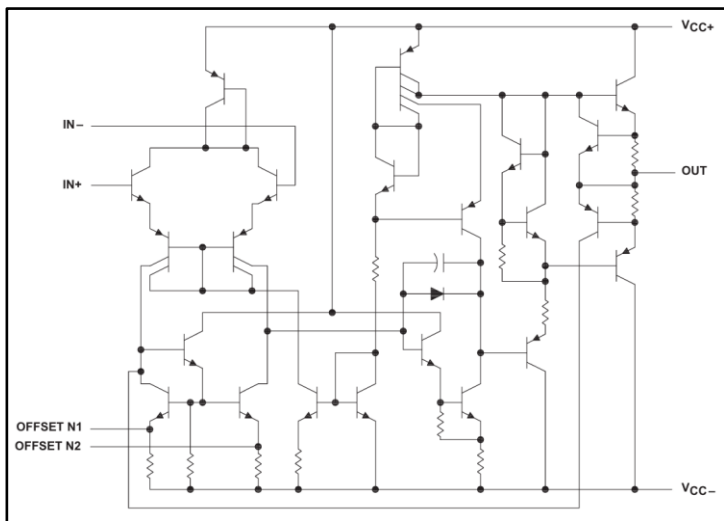Equivalent circuit of Op-Amp
(運算放大器的等效電路)







Component Count	
Transistors	22
Resistors	11
Diode	1
Capacitor	1

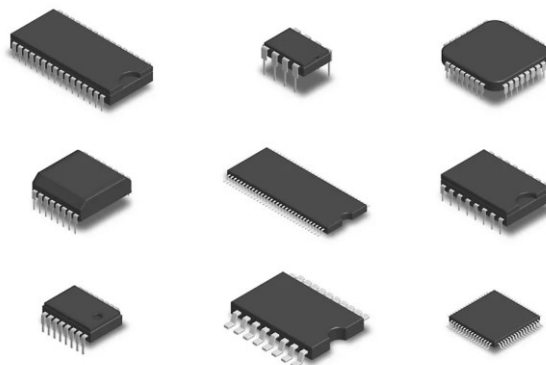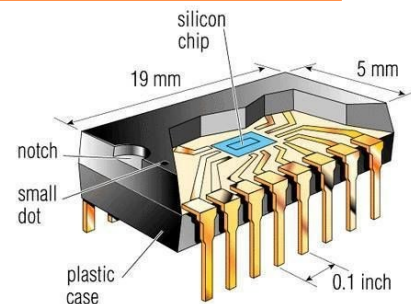


OPERATIONAL AMPLIFIER (OP-AMP)

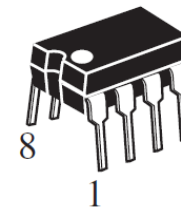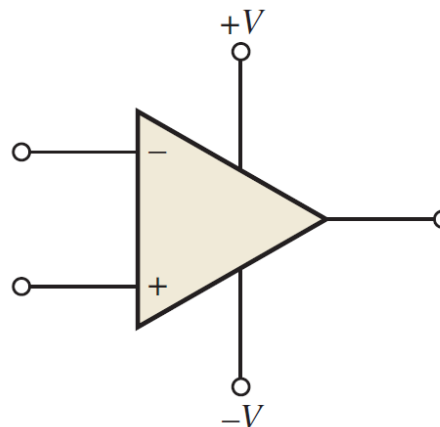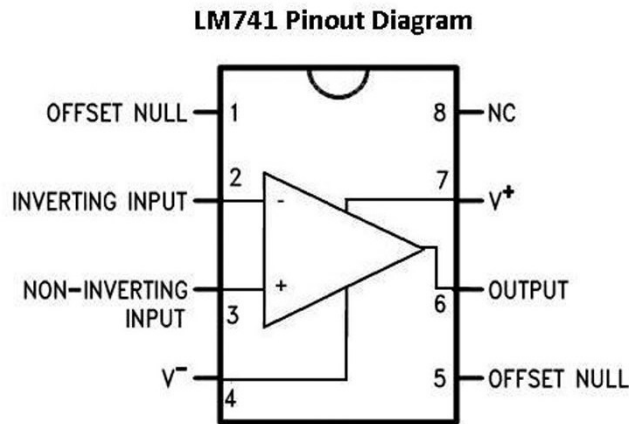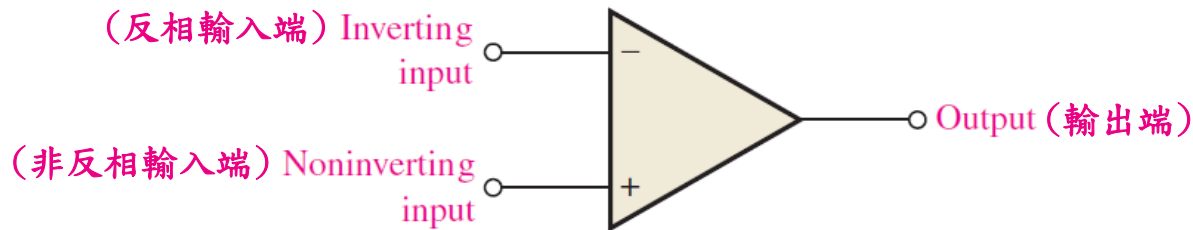
- *Operational Amplifiers (Op-Amp、運算放大器)* are one of the most popular ICs. They have been used to perform mathematical operations 數學運算, such as addition (+), subtraction (-), integration ($\int$), and differentiation (d/dt) – thus the term “*operational* 運算”.




Dual-in line package
(DIP、雙列直插封裝)

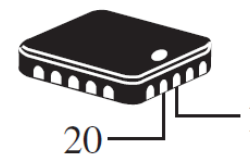

Surface-mount technology
(SMT、表面貼裝技術)

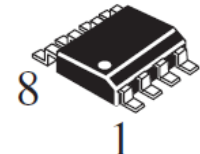

OP-AMP CHARACTERISTICS

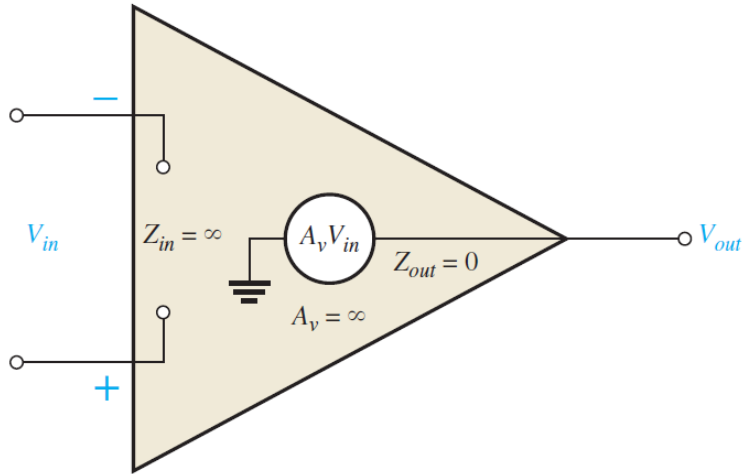


Ideal model

- Infinite input impedance ($Z_{in} = \infty$)
- Zero output impedance ($Z_{out} = 0$)
- Infinite voltage gain ($A_v = \infty$)

$$V_{out} = A_v (V_{in}^+ - V_{in}^-)$$

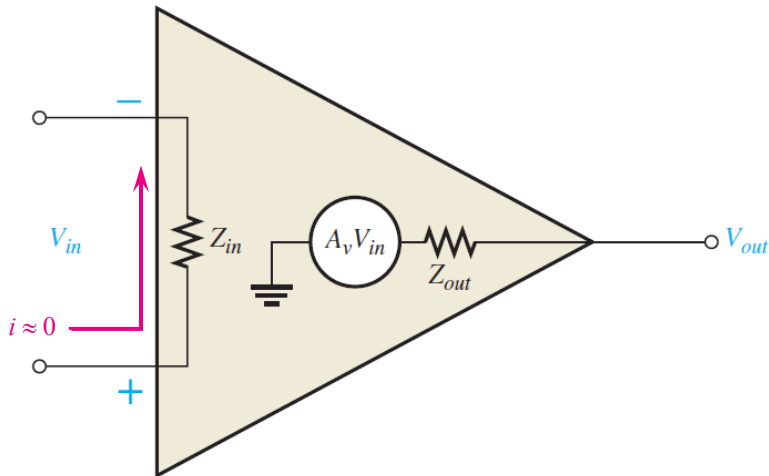"We will use the ideal model in our study"




Practical model

- Very high input impedance ($Z_{in} \rightarrow \infty$)
- Very low output impedance ($Z_{out} \approx 0$)
- Very high voltage gain ($A_v \rightarrow \infty$)
[A_v is typically between 10,000 ~ 500,000]

$$V_{out} \leq A_v (V_{in}^+ - V_{in}^-)$$


OP-AMP INPUT MODES

Single-ended
differential mode
(單端差模)

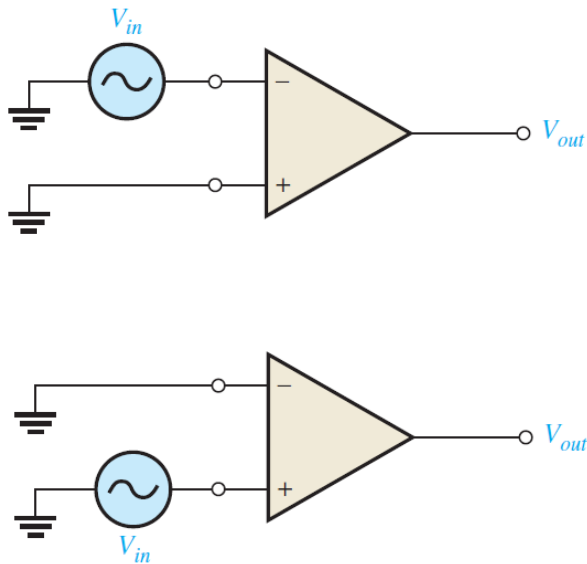


“Amplify the inverted or non-inverted input signal”

Double-ended
differential mode
(雙端差模)

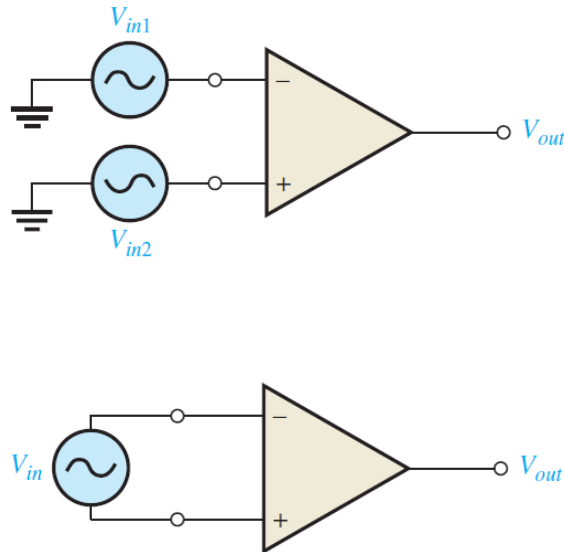

“Amplify the difference between the two inputs”



Common mode
(共模)

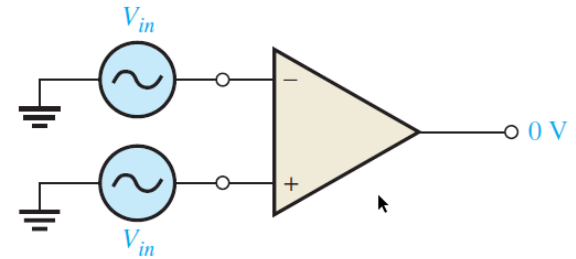


“Cancel out the unwanted signal (noise)”

OPEN-LOOP AND CLOSED-LOOP

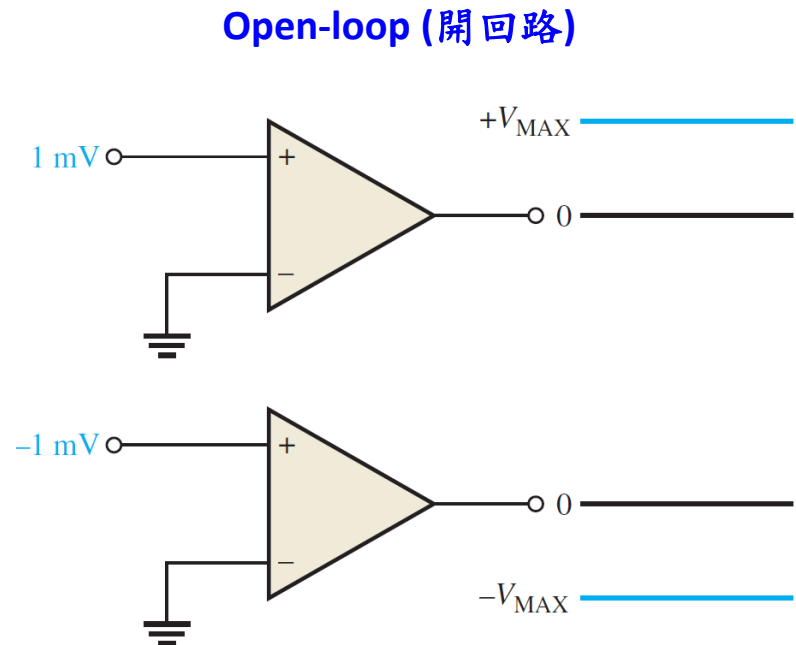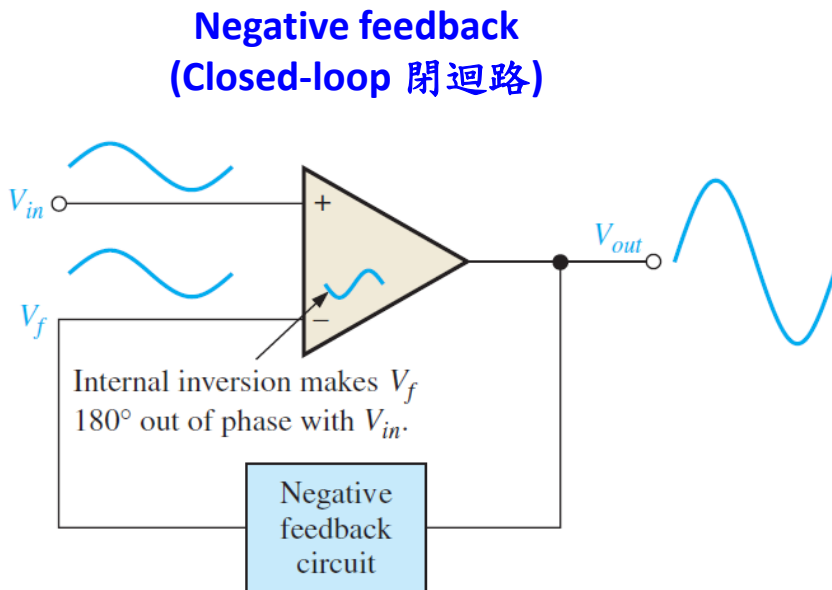- *Op-Amps* have many operational circuits (運算電路), most of which are negative feedback (負回饋) connections.
- If the *Op-Amps* operate with open-loop connection, the application is limited to only comparator (比較器) applications.



NONINVERTING AMPLIFIER 非反相放大器

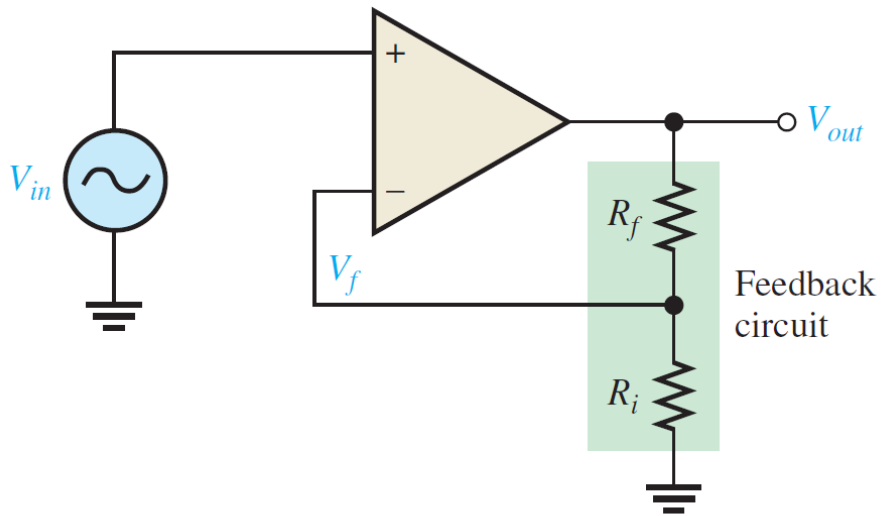

Open-loop gain (A_{ol})

$$V_{out} = A_{ol}(V_{in} - V_f)$$

Open-loop gain (A_{cl})

$$V_{out} = A_{cl}V_{in}$$

A_{ol} is known from the datasheet.
How can we know A_{cl} ?

• Step 1:

$$V_{out} = A_{ol}(V_{in} - V_f) = A_{ol}V_{in} - A_{ol}BV_{out}$$


$$V_f = \underbrace{\frac{R_i}{R_i + R_f}}_B V_{out}$$

• Step 2:

$$\frac{V_{out}}{V_{in}} = \lim_{A_{ol} \rightarrow \infty} \frac{A_{ol}}{1 + A_{ol}B} \cong \frac{A_{ol}}{A_{ol}B} = \frac{1}{B}$$

$$\frac{V_{out}}{V_{in}} = \frac{R_i + R_f}{R_i} = \left(1 + \frac{R_f}{R_i}\right) A_{cl}$$

NONINVERTING AMPLIFIER 非反相放大器

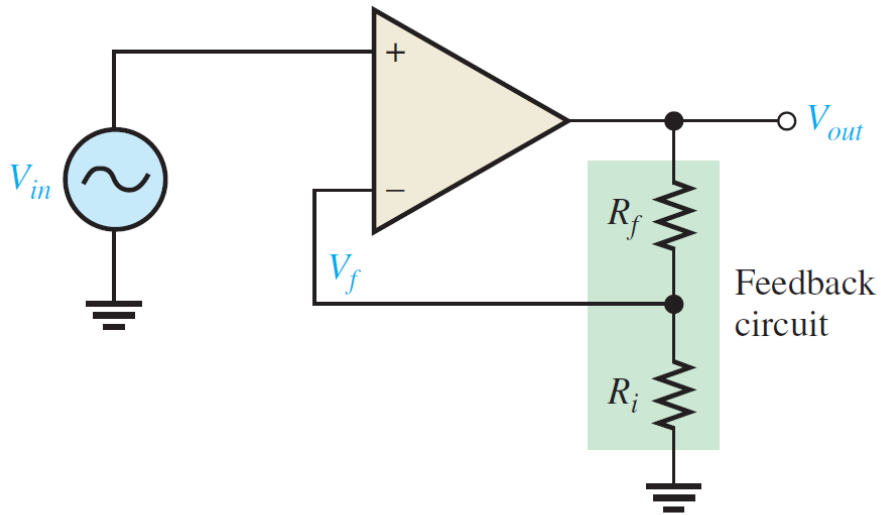


$$\frac{V_{out}}{V_{in}} = \frac{R_i + R_f}{R_i} = 1 + \frac{R_f}{R_i} \left\} A_{cl}$$

$$V_f = \underbrace{\frac{R_i}{R_i + R_f}}_B V_{out} \Rightarrow V_f = V_{in} \quad \text{(Only for negative feedback)}$$

- Simple derivation:


$$V_{in} = \frac{R_i}{R_i + R_f} V_{out} \rightarrow V_{out} = \frac{R_i + R_f}{R_i} V_{in} = \underbrace{\left(1 + \frac{R_f}{R_i}\right)}_{A_{cl}} V_{in} \rightarrow A_{cl} = 1 + \frac{R_f}{R_i}$$

EXERCISE

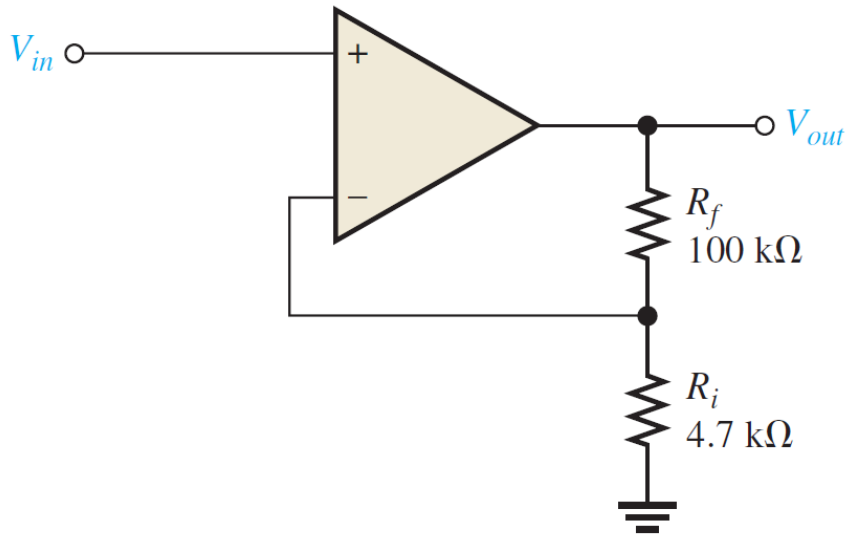


1. Find the closed-loop gain A_{cl} ?
2. If $V_{in} = 0.5$ V, what is V_{out} ?

VOLTAGE-FOLLOWER 電壓隨耦器

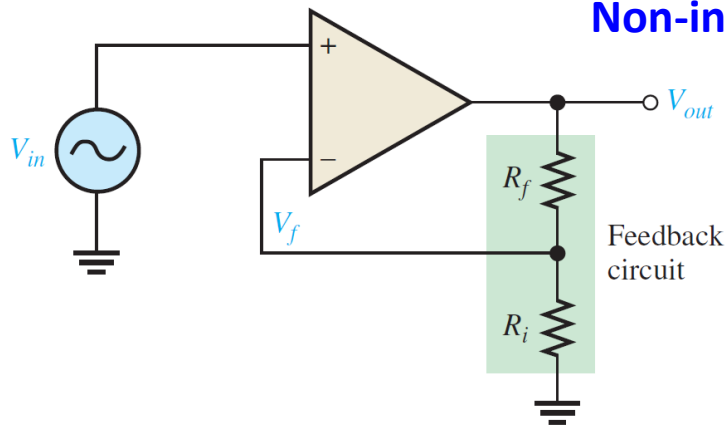
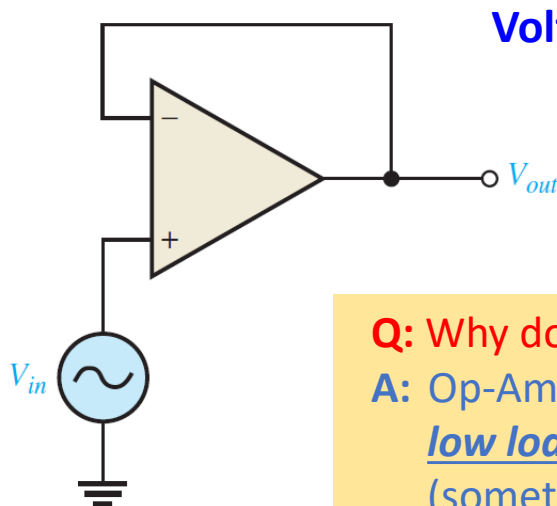
$$\frac{V_{out}}{V_{in}} = 1 + \frac{R_f}{R_i} \Bigg\} A_{cl}$$




$$A_{cl} = \frac{V_{out}}{V_{in}} = 1$$

Q: Why do we need the **voltage-follower**?

A: Op-Amp has high input impedance 輸入阻抗, leading to low load 負載 during signal measurement.
(sometimes called a buffer 緩衝放大器)


INVERTING AMPLIFIER 反相放大器

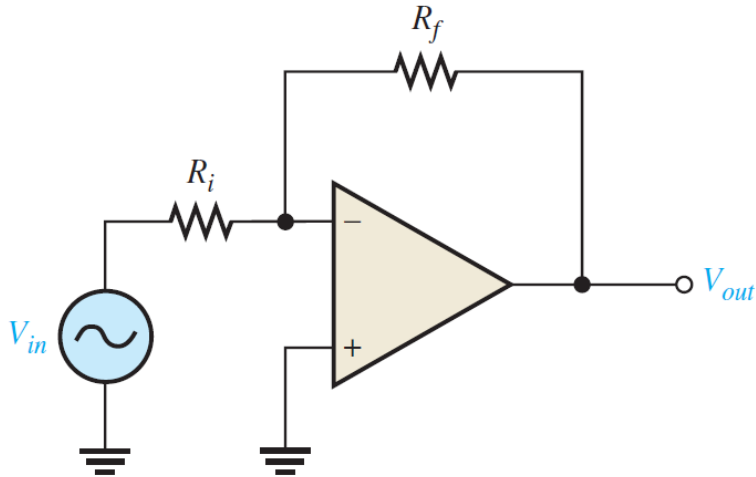

- Find the closed-loop gain A_{cl}


$$A_{cl} = \frac{V_{out}}{V_{in}} = -\frac{R_f}{R_i}$$

EXERCISE

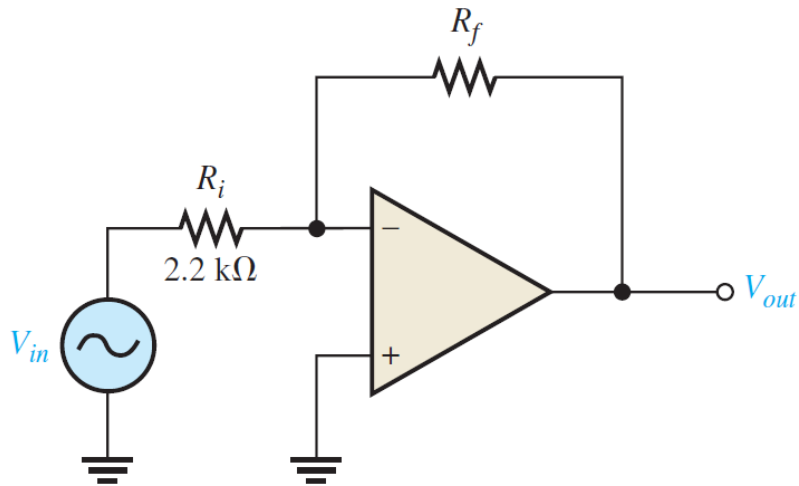


- Determine the value of R_f such that the gain $A_{cl} = -100$.

INPUT AND OUTPUT IMPEDANCE 輸入出阻抗

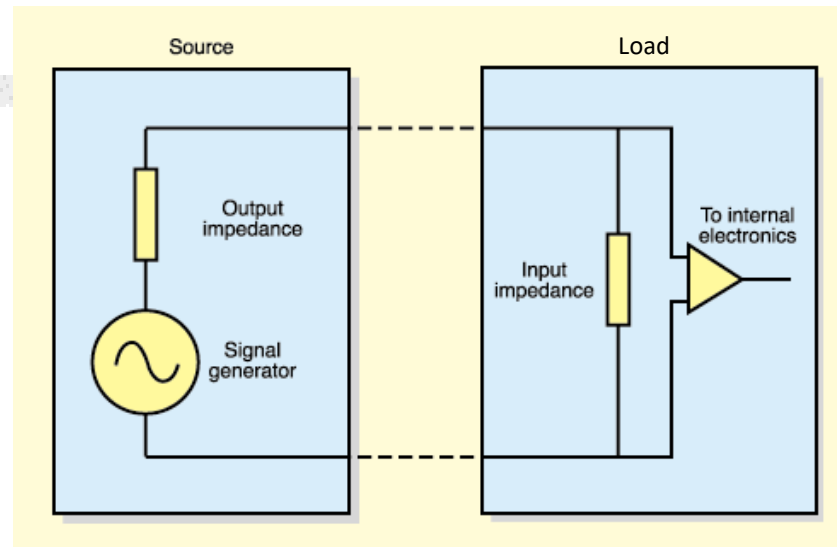

- **Input impedance 輸入阻抗** – the impedance seen by the source, i.e., how much current the input will draw from the source.
 - High input imp. (or low load) – the load draws very little current, not affecting the source.
 - Low input imp. (or high load) – the load draw high current, causing the voltage drop at the source.
- **Output impedance 輸出阻抗** – the impedance seen by the load, i.e., how much the source resists to supply current.
 - High output imp. – the output voltage drops when a load is connected.
 - Low output imp. – the output voltage remains the same, despite heavy load.

I/O IMPEDANCE OF NONINVERTING AMPLIFIER

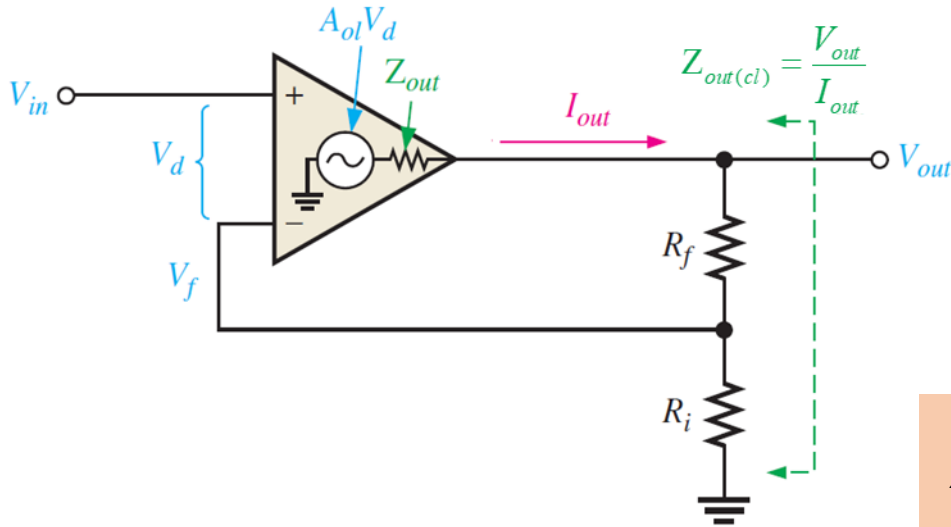

Input impedance analysis

$$B = \frac{R_i}{R_f + R_i}$$

$$V_{in} = V_d + V_f$$

$$V_{in} = V_d + BV_{out} = V_d + A_{ol}BV_d = (1 + A_{ol}B)V_d$$

$$V_{in} = (1 + A_{ol}B)I_{in}Z_{in}$$

$$Z_{in(cl)} = \frac{V_{in}}{I_{in}} = (1 + A_{ol}B)Z_{in}$$


Output impedance analysis

$$V_{out} = A_{ol}V_d - I_{out}Z_{out} = A_{ol}(V_{in} - BV_{out}) - I_{out}Z_{out}$$


$$V_{out} = \frac{A_{ol}V_{in} - I_{out}Z_{out}}{1 + A_{ol}B} \rightarrow Z_{out(cl)} = \left| \frac{dV_{out}}{dI_{out}} \right| = \frac{Z_{out}}{1 + A_{ol}B}$$

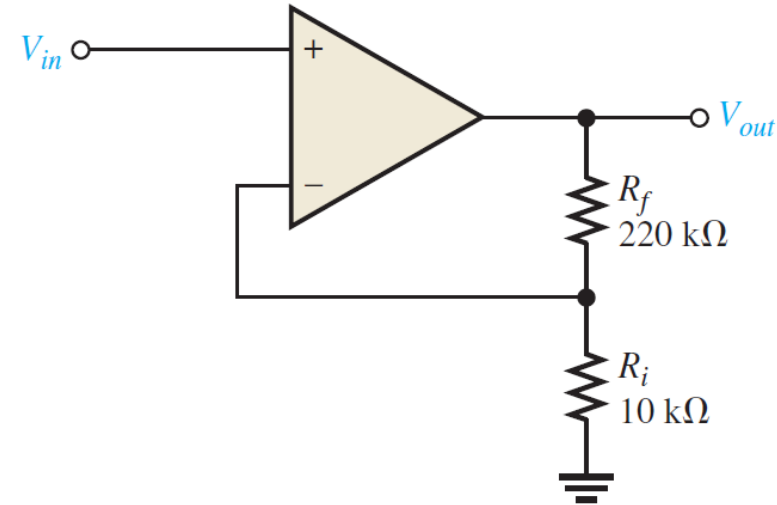EXERCISE

- The Op-Amp datasheet gives $Z_{in} = 2 \text{ M}\Omega$, $Z_{out} = 75 \text{ }\Omega$, and $A_{ol} = 200,000$.
- Determine $Z_{in(cl)}$ and $Z_{out(cl)}$.
 - Find the closed-loop gain A_{cl}



I/O IMPEDANCE OF VOLTAGE-FOLLOWER

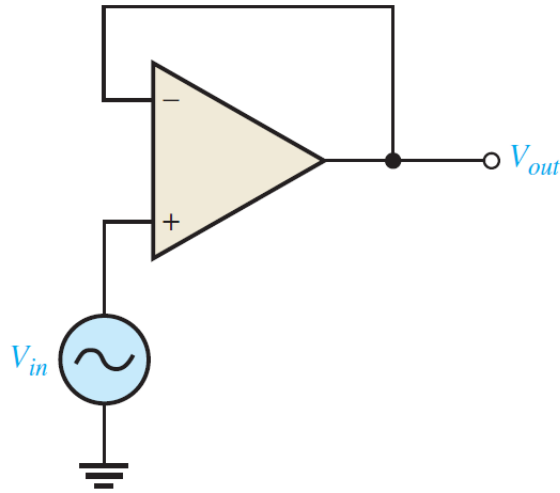

Input impedance analysis

$$Z_{in(cl)} = \frac{V_{in}}{I_{in}} = (1 + A_{ol}B)Z_{in}$$

$$B = \frac{R_i}{R_f + R_i} = 1$$



$$Z_{in(cl)} = (1 + A_{ol})Z_{in}$$

Output impedance analysis

$$Z_{out(cl)} = \frac{Z_{out}}{1 + A_{ol}B}$$

$$Z_{out(cl)} = \frac{Z_{out}}{1 + A_{ol}}$$

I/O IMPEDANCE OF INVERTING AMPLIFIER

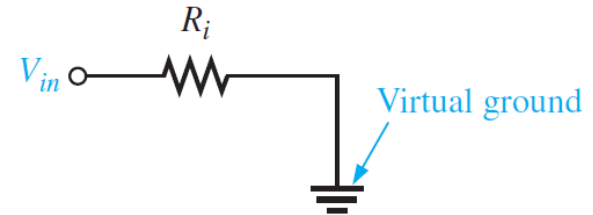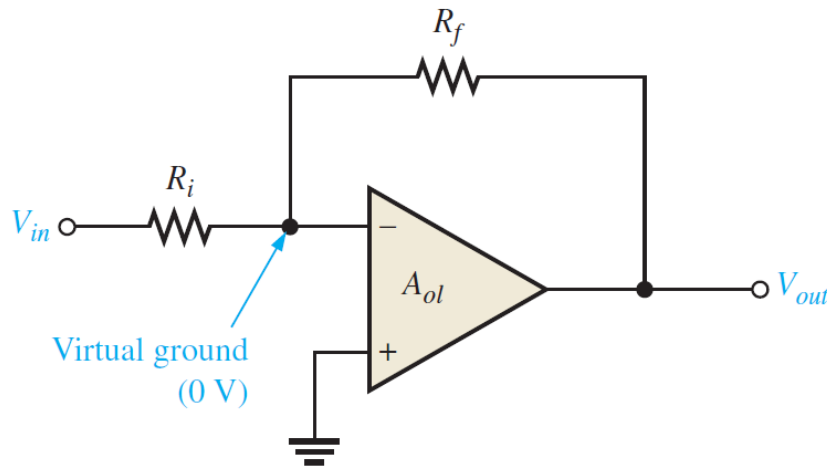

Input impedance analysis

$$Z_{in(cl)} \cong R_i$$

Output impedance analysis

$$V_{out} = A_{ol}V_d - I_{out}Z_{out} = -A_{ol}V_f - I_{out}Z_{out}$$


$$V_{out} = -A_{ol}[BV_{out} + (1-B)V_{in}] - I_{out}Z_{out}$$

$$V_{out} = \frac{-A_{ol}(1-B)V_{in} - I_{out}Z_{out}}{1 + A_{ol}B} \rightarrow Z_{out(cl)} = \left| \frac{dV_{out}}{dI_{out}} \right| = \frac{Z_{out}}{1 + A_{ol}B}$$

(same as the noninverting amplifier)

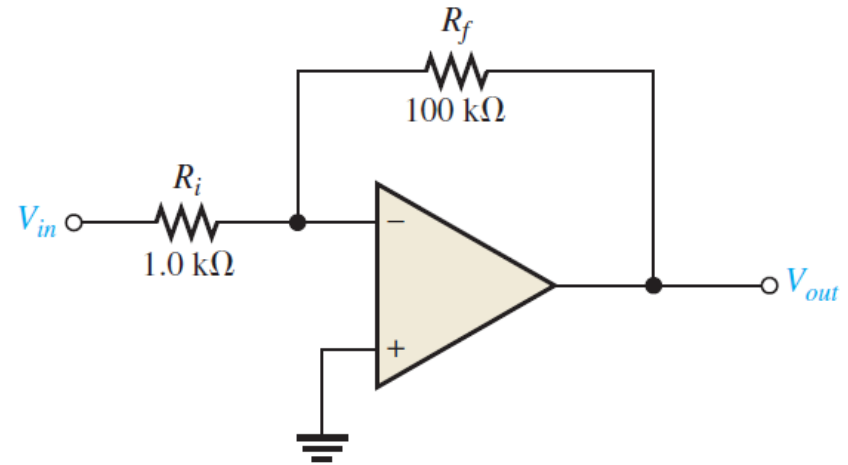EXERCISE

- The Op-Amp datasheet gives $Z_{in} = 4 \text{ M}\Omega$, $Z_{out} = 50 \text{ }\Omega$, and $A_{ol} = 50,000$.
- Determine $Z_{in(cl)}$ and $Z_{out(cl)}$.
 - Find the closed-loop gain A_{cl}



μA741 General-Purpose Operational Amplifiers

1 Features

- Short-Circuit Protection
- Offset-Voltage Null Capability
- Large Common-Mode and Differential Voltage Ranges
- No Frequency Compensation Required
- No Latch-Up

2 Applications

- DVD Recorders and Players
- Pro Audio Mixers

3 Description

The μA741 device is a general-purpose operational amplifier featuring offset-voltage null capability.

The high common-mode input voltage range and the absence of latch-up make the amplifier ideal for voltage-follower applications. The device is short-circuit protected and the internal frequency compensation ensures stability without external components. A low-value potentiometer may be connected between the offset null inputs to null out the offset voltage as shown in [Figure 12](#).


The μA741C device is characterized for operation from 0°C to 70°C.

Device Information⁽¹⁾


PART NUMBER	PACKAGE	BODY SIZE (NOM)
μA741CD	SOIC (8)	4.90 mm × 3.91 mm
μA741CP	PDIP (8)	9.81 mm × 6.35 mm
μA741CPS	SO (8)	6.20 mm × 5.30 mm

(1) For all available packages, see the orderable addendum at the end of the data sheet.

Simplified Schematic

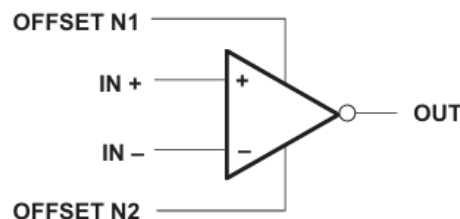

5 Pin Configurations and Functions

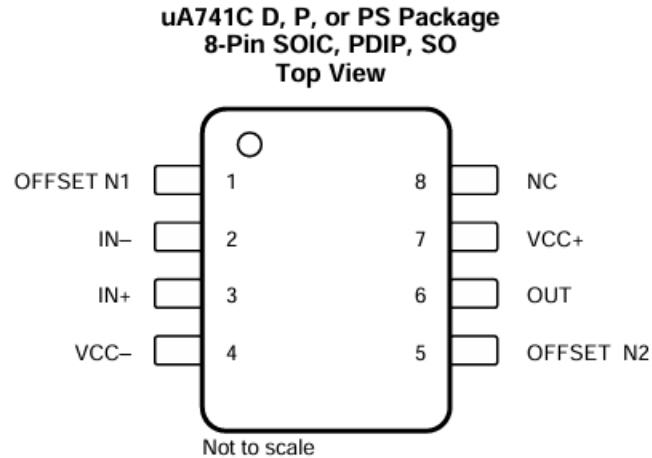

NC- no internal connection

Pin Functions

PIN		I/O	DESCRIPTION
NAME	NO.		
IN+	3	I	Noninverting input
IN-	2	I	Inverting input
NC	8	—	No internal connection
OFFSET N1	1	I	External input offset voltage adjustment
OFFSET N2	5	I	External input offset voltage adjustment
OUT	6	O	Output
VCC+	7	—	Positive supply
VCC-	4	—	Negative supply

6.1 Absolute Maximum Ratings

over virtual junction temperature range (unless otherwise noted)⁽¹⁾

			MIN	MAX	UNIT
Supply voltage, $V_{CC}^{(2)}$	$\mu A741C$		-18	18	V
Differential input voltage, $V_{ID}^{(3)}$	$\mu A741C$		-15	15	V
Input voltage, V_I (any input) ⁽²⁾⁽⁴⁾	$\mu A741C$		-15	15	V
Voltage between offset null (either OFFSET N1 or OFFSET N2) and V_{CC-}	$\mu A741C$		-15	15	V
Duration of output short circuit ⁽⁵⁾			Unlimited		
Continuous total power dissipation			See Thermal Information		
Case temperature for 60 seconds	$\mu A741C$		N/A	N/A	°C
Lead temperature 1.6 mm (1/16 inch) from case for 60 seconds	$\mu A741C$		N/A	N/A	°C
Lead temperature 1.6 mm (1/16 inch) from case for 10 seconds	D, P, or PS package	$\mu A741C$		260	°C
Operating junction temperature, T_J				150	°C
Storage temperature range, T_{stg}	$\mu A741C$		-65	150	°C

6.2 Recommended Operating Conditions

			MIN	MAX	UNIT
V_{CC+} — Supply voltage			5	15	V
	V_{CC-}		-5	-15	
T_A — Operating free-air temperature	$\mu A741C$		0	70	°C


6.4 Electrical Characteristics: $\mu\text{A}741\text{C}$

at specified virtual junction temperature, $V_{\text{CC}\pm} = \pm 15 \text{ V}$ (unless otherwise noted)


PARAMETER		TEST CONDITIONS ⁽¹⁾		MIN	TYP	MAX	UNIT
V_{IO}	Input offset voltage	$V_{\text{O}} = 0$	25°C		1	6	mV
			Full range			7.5	
$\Delta V_{\text{IO(adj)}}$	Offset voltage adjust range	$V_{\text{O}} = 0$	25°C		± 15		mV
I_{IO}	Input offset current	$V_{\text{O}} = 0$	25°C		20	200	nA
			Full range			300	
I_{IB}	Input bias current	$V_{\text{O}} = 0$	25°C		80	500	nA
			Full range			800	
V_{ICR}	Common-mode input voltage range	25°C		± 12	± 13		V
		Full range		± 12			
V_{OM}	Maximum peak output voltage swing	$R_{\text{L}} = 10 \text{ k}\Omega$	25°C	± 12	± 14		V
		$R_{\text{L}} \geq 10 \text{ k}\Omega$	Full range	± 12			
		$R_{\text{L}} = 2 \text{ k}\Omega$	25°C	± 10			
		$R_{\text{L}} \geq 2 \text{ k}\Omega$	Full range	± 10			
A_{VD}	Large-signal differential voltage amplification	$R_{\text{L}} \geq 2 \text{ k}\Omega$	25°C	20	200		V/mV
		$V_{\text{O}} = \pm 10 \text{ V}$	Full range	15			
r_{i}	Input resistance	25°C		0.3	2		M Ω
r_{o}	Output resistance	$V_{\text{O}} = 0$; see ⁽²⁾	25°C		75		Ω
C_{i}	Input capacitance	25°C			1.4		pF
CMRR	Common-mode rejection ratio	$V_{\text{IC}} = V_{\text{ICRmin}}$	25°C	70	90		dB
			Full range	70			
k_{SVS}	Supply voltage sensitivity ($\Delta V_{\text{IO}}/\Delta V_{\text{CC}}$)	$V_{\text{CC}} = \pm 9 \text{ V to } \pm 15 \text{ V}$	25°C		30	150	$\mu\text{V/V}$
			Full range			150	
I_{OS}	Short-circuit output current	25°C			± 25	± 40	mA
I_{CC}	Supply current	$V_{\text{O}} = 0$; no load	25°C		1.7	2.8	mA
			Full range			3.3	
P_{D}	Total power dissipation	$V_{\text{O}} = 0$; no load	25°C		50	85	mW
			Full range			100	

SUMMARY

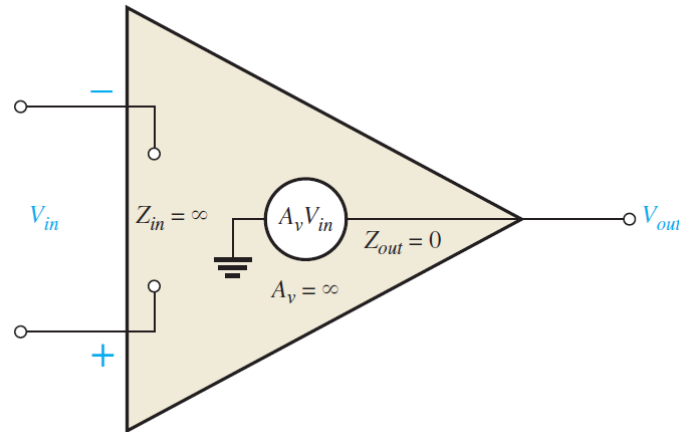- Op-Amp have
 1. High input impedance
 2. Low output impedance
 3. High voltage gain



Non-inverting amplifier

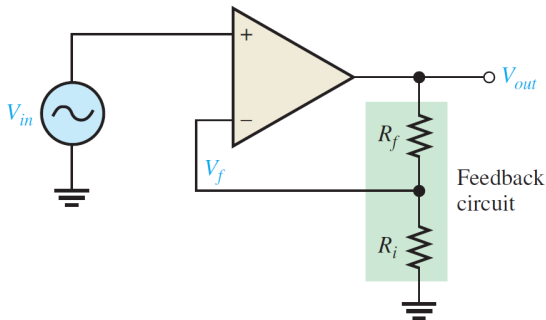


$$A_{cl} = 1 + \frac{R_f}{R_i}$$

$$Z_{in(cl)} = (1 + A_{ol}B)Z_{in}$$

$$Z_{out(cl)} = \frac{Z_{out}}{1 + A_{ol}B}$$

Voltage-follower

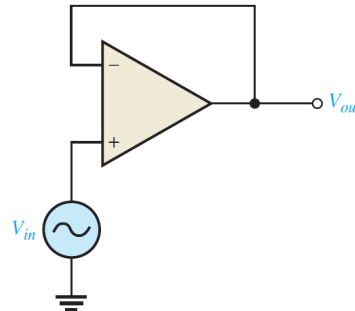


$$A_{cl} = \frac{V_{out}}{V_{in}} = 1$$

$$Z_{in(cl)} = (1 + A_{ol})Z_{in}$$

$$Z_{out(cl)} = \frac{Z_{out}}{1 + A_{ol}}$$

Inverting amplifier

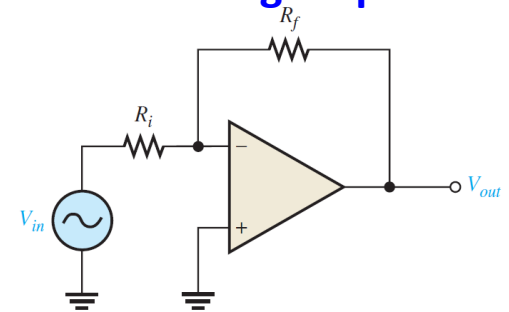

$$A_{cl} = -\frac{R_f}{R_i}$$

$$Z_{in(cl)} \cong R_i$$

$$Z_{out(cl)} = \frac{Z_{out}}{1 + A_{ol}B}$$